
CMPEN 411

VLSI Digital Circuits

Spring 2012

Lecture 13: Designing for Low Power

[Adapted from Rabaey's *Digital Integrated Circuits*, Second Edition, ©2003
J. Rabaey, A. Chandrakasan, B. Nikolic]

Review: Designing Fast CMOS Gates


- ❑ Transistor sizing
 - fet closest to the output is smallest of series fets
- ❑ Transistor ordering
 - put latest arriving signal closest to the output
- ❑ Logic structure reordering
 - replace large fan-in gates with smaller fan-in gate network
- ❑ Logical effort
- ❑ Buffer (inverter) insertion
 - separate large fan-in from large C_L with buffers
 - uses buffers so that the path delay is minimized

Why Power Matters

- ❑ Packaging costs
- ❑ Power supply rail design
- ❑ Chip and system cooling costs
- ❑ Noise immunity and system reliability
- ❑ Battery life (in portable systems)
- ❑ Environmental concerns
 - Office equipment accounted for 5% of total US commercial energy usage in 1993
 - *Energy Star* compliant systems

Why worry about power? – Power Dissipation

 
Lead microprocessors power continues to increase



Power delivery and dissipation will be prohibitive

Source: Borkar, De Intel®

 
Why worry about power? – Chip Power Density




Source: Borkar, De Intel®

Chip Power Density Distribution => Heat

Power Map

 

On-Die Temperature

 

- ❑ Heat dissipation => temperature,
higher power density => higher temperature
 - ❑ Power density is not uniformly distributed across the chip
- Intel Pentium 4: (0.18 μm) 64 W @ 217 mm^2
- Intel Pentium 4: (90 nm) 103W @ 112 mm^2

Examples



Apple Power G5



Problem Illustration

***What happens
when the
CPU cooler is
removed?***



www.tomshardware.de
www.tomshardware.com

Power and temperature are BAD

❑ and can be EVIL



Source: Tom's Hardware Guide

<http://www6.tomshardware.com/cpu/01q3/010917/heatvideo-01.html>

Power and Energy Figures of Merit

❑ Power consumption in Watts

- determines battery life in hours

❑ Peak power

- determines power ground wiring designs
- sets packaging limits
- impacts signal noise margin and reliability analysis



❑ Energy efficiency in Joules

- rate at which power is consumed over time

❑ Energy = power * delay

- Joules = Watts * seconds
- lower energy number means less power to perform a computation at the same frequency


Power versus Energy

  

PDP and EDP

- ❑ Power-delay product (**PDP**) = $P_{av} * t_p = (C_L V_{DD}^2)/2$
 - PDP is the average **energy** consumed per switching event (Watts * sec = Joule)
 - **lower** power design could simply be a **slower** design
- ❑ Energy-delay product (**EDP**) = $PDP * t_p = P_{av} * t_p^2$

 
- EDP is the average **energy** consumed multiplied by the computation time required
- takes into account that one can **trade** increased delay for lower energy/operation (e.g., via supply voltage scaling that increases delay, but decreases energy consumption)



- allows one to understand tradeoffs better

Understanding Tradeoffs

 - Which design is the “best” (fastest, coolest, both) ?



CMOS Power Equations


$$P = C_L V_{DD}^2 f + t_{sc} V_{DD} I_{peak} f + V_{DD} I_{leak}$$

Dynamic
power

Short-circuit
power

Leakage
power

Dynamic Power Consumption

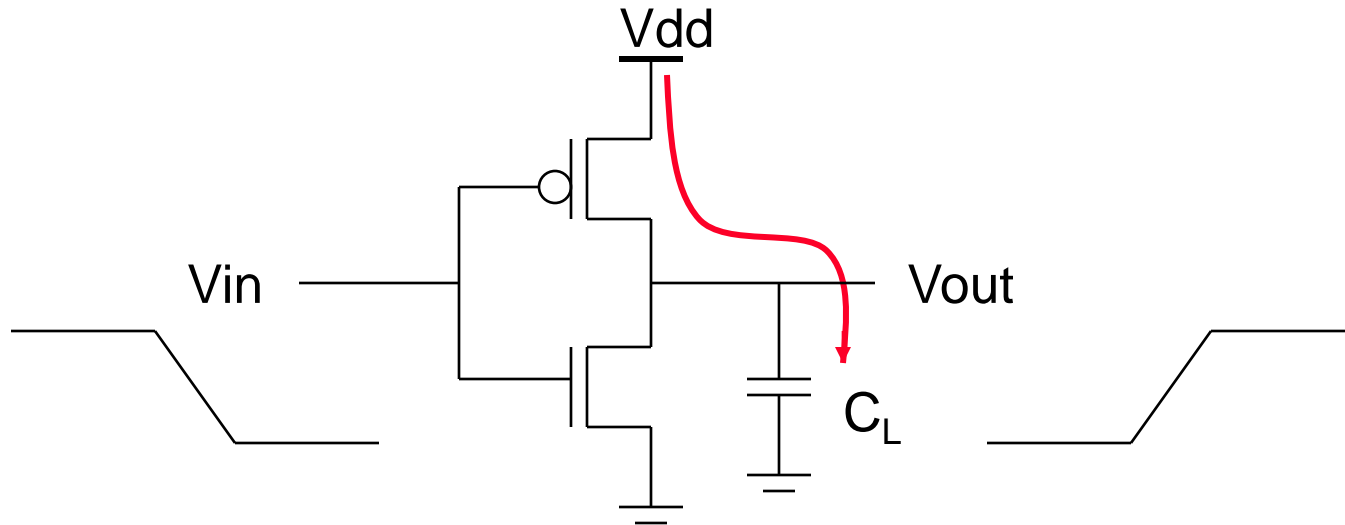

$$\text{Energy/transition} = C_L * V_{DD}^2 * P_{0 \rightarrow 1}$$

$$P_{\text{dyn}} = \text{Energy/transition} * f = C_L * V_{DD}^2 * P_{0 \rightarrow 1} * f$$

$$P_{\text{dyn}} = C_{\text{EFF}} * V_{DD}^2 * f \quad \text{where } C_{\text{EFF}} = P_{0 \rightarrow 1} C_L$$

Not a function of transistor sizes!

Data dependent - a function of **switching activity**!

Lowering Dynamic Power

Capacitance:

Function of fan-out,
wire length, transistor
sizes

Supply voltage:

Has been dropping
with successive
generations

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 P_{0 \rightarrow 1} f$$


Activity factor:

How often, on average,
do wires switch?

Clock frequency:

Increasing...

Short Circuit Power Consumption

 


Finite slope of the input signal causes a direct current path between V_{DD} and GND for a short period of time during switching when both the NMOS and PMOS transistors are conducting.

Short Circuit Currents Determinates

$$P_{sc} = t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1}$$


- ❑ Duration and slope of the input signal, t_{sc}
- ❑ I_{peak} determined by
 - the saturation current of the P and N transistors which depend on their **sizes**, process technology, temperature, etc.
 - strong function of the ratio between input and output slopes
 - a function of C_L

Impact of C_L on P_{sc}

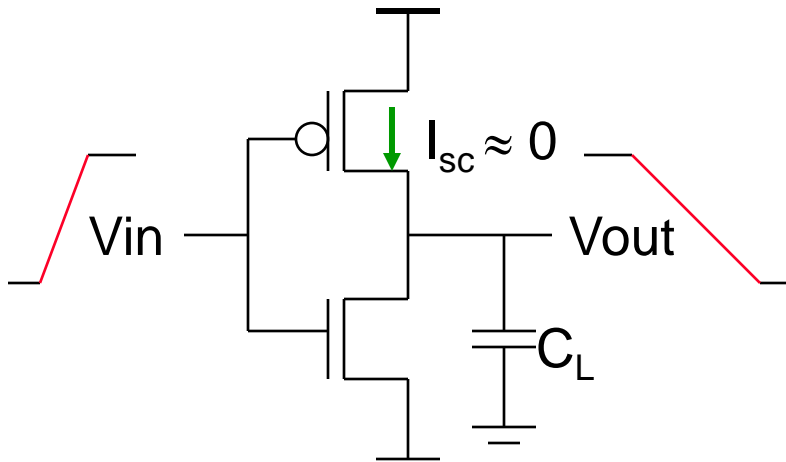

Large capacitive load

 
Output fall time significantly larger than input rise time.



Small capacitive load

Output fall time substantially smaller than the input rise time.

I_{peak} as a Function of C_L

 


When load capacitance is small, I_{peak} is large.

Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - **slope engineering**.

500 psec input slope

P_{sc} as a Function of Rise/Fall Times

 





When load capacitance is small ($t_{sin}/t_{sou} > 2$ for $V_{DD} > 2\text{V}$) the power is dominated by P_{sc}

If $V_{DD} < V_{Tn} + |V_{Tp}|$ then P_{sc} is eliminated since both devices are never on at the same time.


$$\begin{aligned} W/L_p &= 1.125\text{ }\mu\text{m}/0.25\text{ }\mu\text{m} \\ W/L_n &= 0.375\text{ }\mu\text{m}/0.25\text{ }\mu\text{m} \\ C_L &= 30\text{ fF} \end{aligned}$$

normalized wrt zero input
rise-time dissipation

Is Transistor a Good Switch?

    


Leakage (Static) Power Consumption

 

Sub-threshold current is the dominant factor.

Leakage as a Function of V_T

 - Continued scaling of supply voltage and the subsequent scaling of threshold voltage will make subthreshold conduction a dominate component of power dissipation.




- An 90mV/decade V_T roll-off - so each 270mV increase in V_T gives 3 orders of magnitude reduction in leakage (but adversely affects performance)

TSMC Processes Leakage and V_T

	CL018 G	CL018 LP	CL018 ULP	CL018 HS	CL015 HS	CL013 HS
V_{dd}	1.8 V	1.8 V	1.8 V	2 V	1.5 V	1.2 V
T_{ox} (effective)	42 Å	42 Å	42 Å	42 Å	29 Å	24 Å
L_{gate}	0.16 μm	0.16 μm	0.18 μm	0.13 μm	0.11 μm	0.08 μm
I_{DSat} (n/p) ($\mu A/\mu m$)	600/260	500/180	320/130	780/360	860/370	920/400
I_{off} (leakage) ($pA/\mu m$)	20	1.60	0.15	300	1,800	13,000
V_{Tn}	0.42 V	0.63 V	0.73 V	0.40 V	0.29 V	0.25 V
FET Perf. (GHz)	30	22	14	43	52	80

From MPR, 2000

Exponential Increase in Leakage Currents

 


From De,1999

Itanium example


Itanium 2 (Intel)

0.18 um, 1.5V, 1Ghz, 221M transistors

 

Latest generation Itanium (Intel)

0.13 um, 1.3V, 1.5Ghz, 410M transistors

 

example

Next Lecture

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active (Dynamic)	Logic design Reduced V_{dd} TSizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage (Standby)	Multi- V_T Stack effect Pin ordering	Sleep Transistors Multi- V_{dd} Variable V_T Input control	Variable V_T