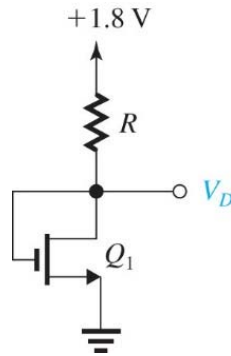


Exercise MOSFET (2)


Problem 1 (*Exercise D5.9 in 7th edition textbook.*)

For the circuit below, find the value of R that results in $V_D = 0.7$ V. The MOSFET has $V_m = 0.5$ V, $\mu_n C_{ox} = 0.4$ mA/V², and $W/L = 0.72$ $\mu\text{m} / 0.18$ μm .



Problem 2 (*Exercise 5.14 in 7th edition textbook.*)

For the circuit below, find the value of R that results in the PMOS transistor operating with an overdrive voltage of $|V_{OV}| = 0.6 \text{ V}$. The threshold voltage is $V_{tp} = -0.4 \text{ V}$, $k'_p = 0.1 \text{ mA/V}^2$, and $W/L = 10 \text{ } \mu\text{m}/0.18 \text{ } \mu\text{m}$.

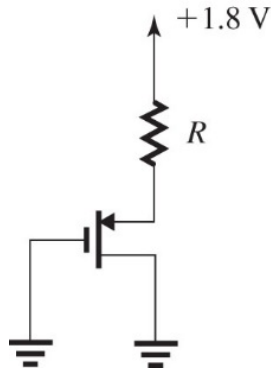

Problem 3 (Problem 5.51 in 7th edition textbook.)

The NMOS transistors in the circuit below have $V_t = 0.5$ V, $\mu_n C_{ox} = 90$ $\mu\text{A}/\text{V}^2$, and $L_1 = L_2 = L_3 = 0.5$ μm . Find the required values of gate width for each of Q_1 , Q_2 , and Q_3 to obtain the voltage and current values indicated.

