



Differential Impedance **...*finally* made simple**

Eric Bogatin

President

Bogatin Enterprises

www.BogatinEnterprises.com

913-393-1305

eric@bogent.com




Overview

- What's impedance
- Differential Impedance: a simple perspective
- Coupled Transmission line formalism
- Measuring differential impedance
- Emulating effects of a split in return path
- Calculating differential impedance

~~Bogatin Enterprises~~
MYTHS

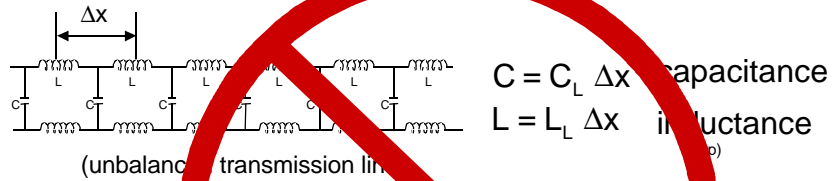First Order Model of a Transmission Line (Loss Less Model)




The circuit analysis result:

$$Z_0 = \sqrt{\frac{L}{C}} \quad TD = \sqrt{L_{\text{total}} C_{\text{total}}} \quad \gamma = \frac{1}{\sqrt{L_L C_L}}$$

~~Bogatin Enterprises~~
MYTHS


“...be the signal”

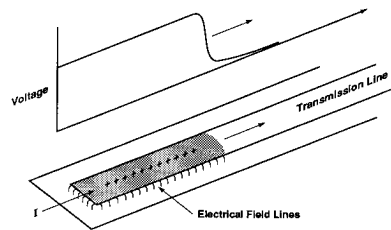

courtesy ICE



0th Order Model of Transmission Line

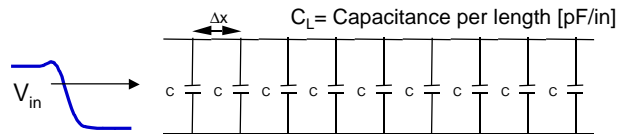

$$C = C_L \Delta x$$

$$\Delta Q = CV,$$

$$\text{every } \Delta t = \frac{\Delta x}{v}$$

I, V definition of Transmission Line:

$$I = \frac{\Delta Q}{\Delta t} = \frac{v C_L \Delta x V}{\Delta x} = v C_L V$$

What's the impedance?



Instantaneous Impedance of a Transmission Line

$$I = v C_L V$$

$$Z = \frac{V}{I} = \frac{V}{v C_L V} = \frac{1}{v C_L}$$


$$Z_0 = \frac{1}{v C_L}$$

Features of the impedance:

- looks like a resistor
- dependant on intrinsic properties only
- is an intrinsic property
- independent of length
- defined as the "characteristic impedance" = Z_0
- also called the "surge impedance" or "wave impedance"



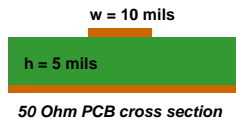Characteristic Impedance and Capacitance per Length



increase h

What happens to the capacitance per length? The characteristic impedance?

increase w


What happens to the capacitance per length? The characteristic impedance?




$$Z_0 \sim \frac{1}{C_L}$$



What Does it Mean to Have a 50 Ohm Line?

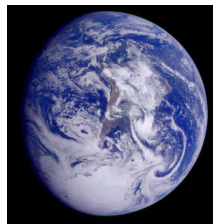

Verrrry longggggg 50 Ohm coax

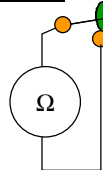

What will Ohm-meter read?

For the first second? After 3 seconds? After 10 sec?



An important Distinction


- **THE** impedance of the transmission line (may be time dependent)
- The **instantaneous** impedance of the transmission line
- The **Characteristic** impedance of the transmission line

Just referring to "...the impedance" may be a bit ambiguous




Return Path in T Lines

Current into signal line

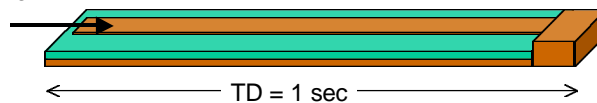

Where is the return path?


For DC currents:

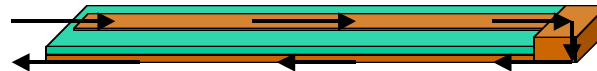

For RF currents? When does current come out return path?



Current Flow in the Transmission Line

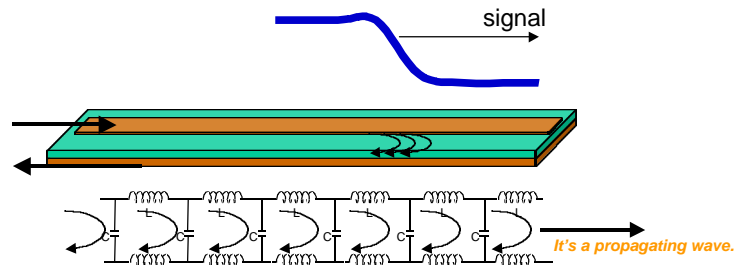

What happens initially if the end is open?, shorted?, terminated?

To control impedance, manage the return path as carefully as the signal path



The Growing Importance of Differential Pair Use


Early Applications for Differential Pairs

MECL I	1962
MECL II	1966
MECL III	1968
MECL 10k	1979
MECL 10kH	1981

ANSI/TIA/EIA-644-1995 is the generic physical layer standard for LVDS. It was approved in November of 1995, and first published in March of 1996.

Example: high speed serial transmission

TI 1.8 Gbps LVDS TRX

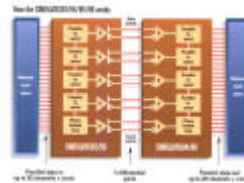

→ IEEE1394
→ IEEE488
→ Gigabit Ethernet




What's a Differential Pair Transmission Line?

???



What's a Differential Pair Transmission Line?

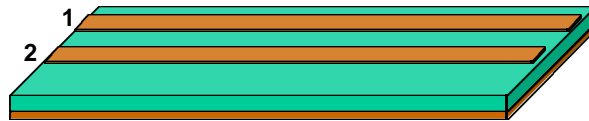Answer:any two, coupled transmission lines (with their return paths).




A special case: a symmetric pair

What's differential impedance?


Bogatin Enterprises
MYTHS

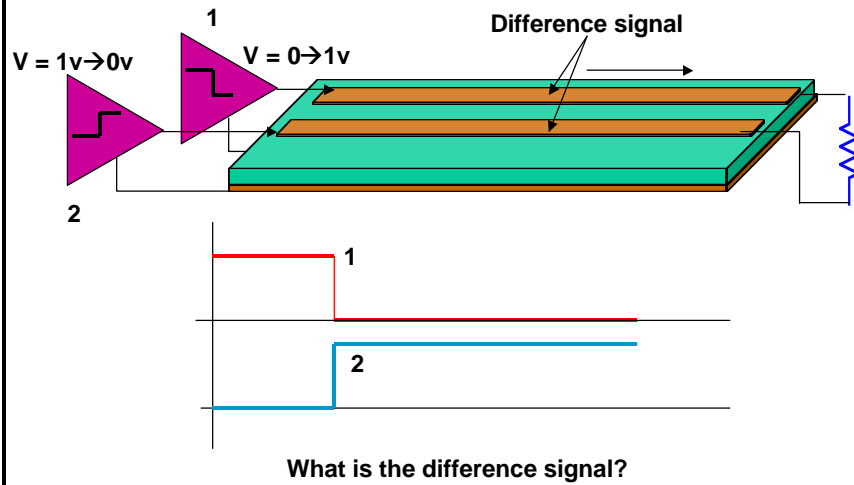Differentially Driving a Differential Pair



Bogatin Enterprises
MYTHS

The Difference Signal

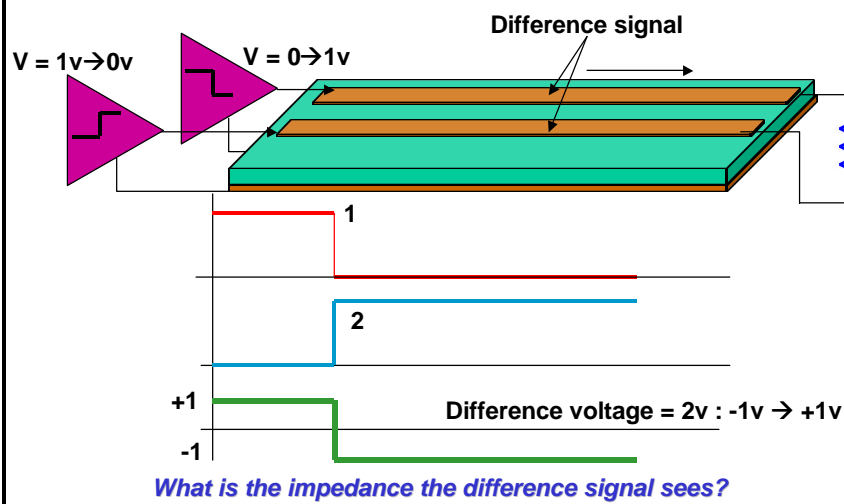




Differential Impedance

Differential Impedance: the impedance the difference signal sees

$$Z(\text{diff}) = \frac{V(\text{diff})}{I_{\text{one}}} = \frac{2V}{I_{\text{one}}} \approx 2(Z_0 - \text{small})$$

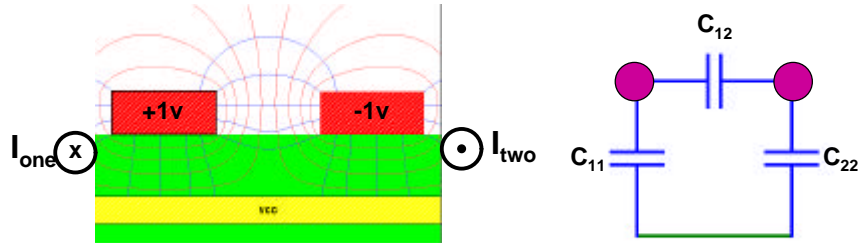Differential impedance decreases as coupling increases





How will the capacitance matrix elements be affected by spacing?

© Eric Bogatin 2000

www.BogatinEnterprises.com



Capacitance Matrix Elements

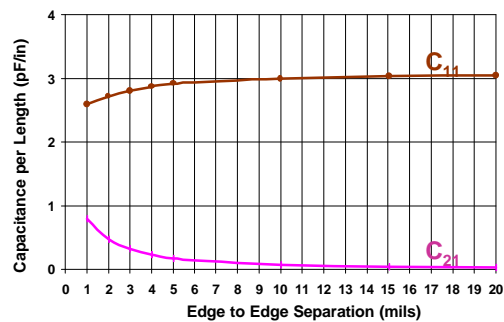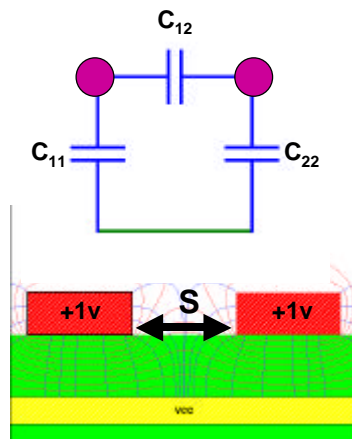


What happens to the differential impedance as S gets smaller?

© Eric Bogatin 2000

www.BogatinEnterprises.com




How to Terminate the Difference Signal?

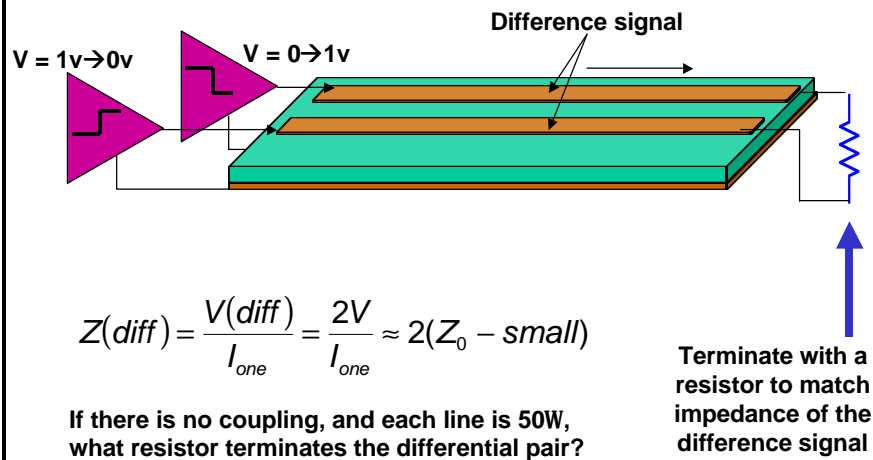


Formalism: Mode Pattern for Identical Traces

Hyperlynx simulation

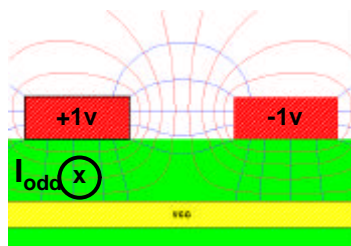

Corresponds to differential driven

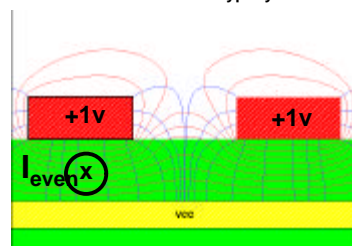


Corresponds to common driven

What is I_{odd} compared to I_{even} ?
How do they vary with spacing?




Odd and Even Mode Impedance

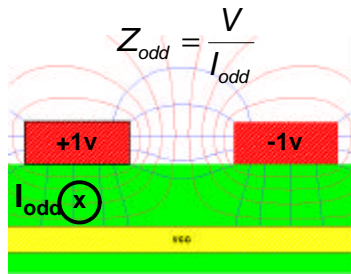

Mode: odd, or 1, or a

Odd mode current increases as traces are brought together

Odd mode impedance decreases

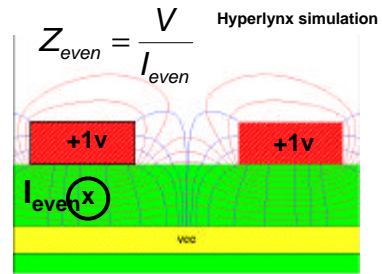


Mode: even, or 2, or b

Even mode current decreases as traces are brought together

Even mode impedance increases



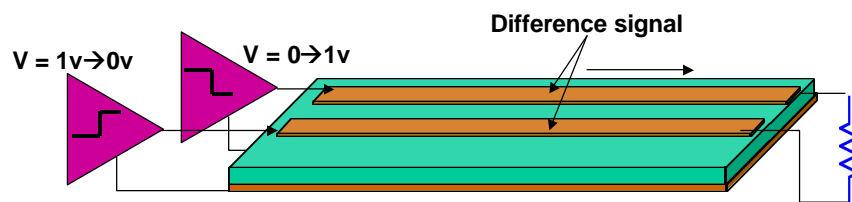
Differential Impedance and Odd Mode Impedance



$$Z(\text{diff}) = \frac{V(\text{diff})}{I_{\text{one}}} = \frac{2V}{I_{\text{one}}} = 2 \times Z_{\text{odd}}$$



The Characteristic Impedance Matrix

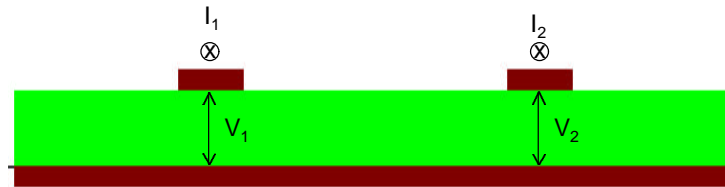


Define a Characteristic Impedance Matrix

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{22}I_2 + Z_{21}I_1$$

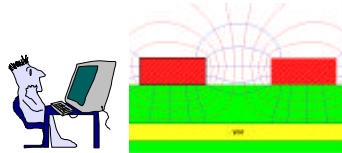How is Z_{12} influenced by coupling?
Is Z_{12} large or small?



Characteristic Impedance Matrix [ohms]:

	1	2
1	49.6	6.4
2	6.4	49.6

Hyperlynx simulation



Definition of Odd and Even Mode Impedance

(Special case: symmetric)



$$V_{odd} = \frac{1}{2}(V_1 - V_2)$$

$$Z_{odd} = \left. \frac{V_{odd}}{I_1} \right|_{V_{even}=0}$$

Define:

$$V_{even} = \frac{1}{2}(V_1 + V_2)$$

$$Z_{even} = \left. \frac{V_{even}}{I_1} \right|_{V_{odd}=0}$$

What is the voltage when $V_{even} = 0$? When $V_{odd} = 0$?



Odd and Even Mode Impedance

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{22}I_2 + Z_{21}I_1$$

Odd Mode: $I_1 = -I_2$ $V_{odd} = \frac{1}{2}(V_1 - V_2) = (Z_{11} - Z_{12})I_1$

$$Z_{odd} = (Z_{11} - Z_{12})$$

Odd mode impedance is reduced with coupling

Even Mode: $I_1 = I_2$ $V_{even} = \frac{1}{2}(V_1 + V_2) = (Z_{11} + Z_{12})I_1$

$$Z_{even} = Z_{11} + Z_{12}$$

Even mode impedance is increased with coupling



Mode Impedances

Odd mode impedance is the impedance of one line when the pair is driven differentially

$$Z_{odd} = (Z_{11} - Z_{12})$$

Differential impedance: $Z(diff) = \frac{V(diff)}{I} = \frac{2V}{I} = 2(Z_{odd}) = 2(Z_{11} - Z_{12})$

Even mode impedance is the impedance of one line when the pair is driven commonly

$$Z_{even} = Z_{11} + Z_{12}$$

Common impedance: $Z_{common} = Z_{even} = Z_{11} + Z_{12}$



Summary So Far

- A differential pair is any two transmission lines
- Special case: symmetric lines
- Differential driving has symmetric, opposite signal on each line
- Differential impedance is the impedance the difference signal sees
- With no coupling, current into one line depends on capacitance per length of the line
- With coupling, current into one line depends on how the other line is driven
- The impedance of one line will depend on how the other line is driven

The differential impedance will be twice the impedance of one line when the pair is driven differentially



How can differential impedance be measured?



TDR Equipment

HP 83480A
Digital Communications Analyzer
(mainframe)

TDR: Time Domain Reflection
TDT: Time Domain Transmission
DTDR: Differential Time Domain Reflection
DTDT: Differential Time Domain Transmission




HP 54754A
Differential TDR Module
Two independent TDR channels
- simultaneous TDR/TDT
- simultaneous differential TDR

HP 83484A
2 Channel 50 GHz Module
Two independent voltage channels




Conventional Single Channel TDR

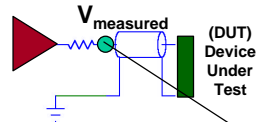TDR: 400 mV output, unloaded
50W output impedance




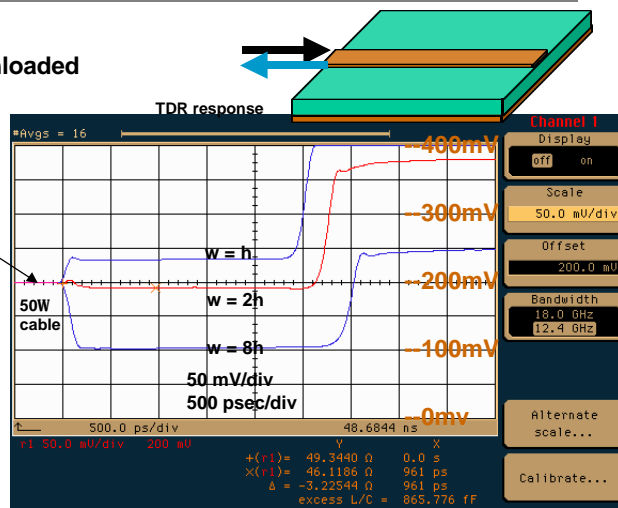3 different line width microstrips,
each 9 inches long





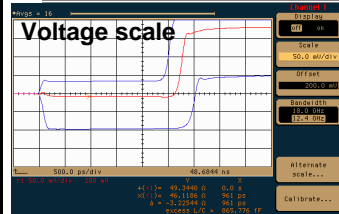Converting Reflected Voltage into Impedance




$$\rho = \frac{V_{\text{reflected}}}{V_{\text{incident}}}$$

$$Z_{DUT} = 50\Omega \frac{1-\rho}{1+\rho}$$

Plotting
impedance
directly

70W
60W
50W
40W
30W
20W

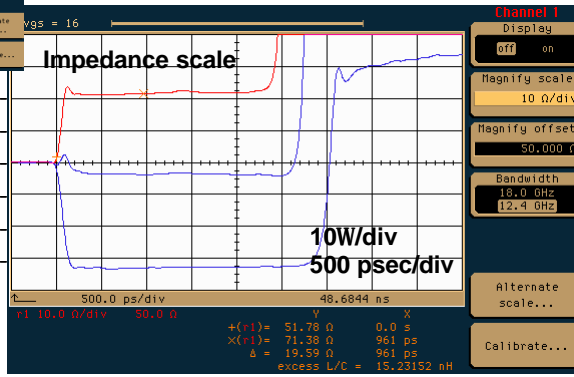


© Eric Bogatin 2000




www.BogatinEnterprises.com


Two Channel Differential TDR: Differential or Common Driven

Driving differential signal

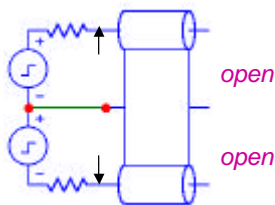

Driving common signal

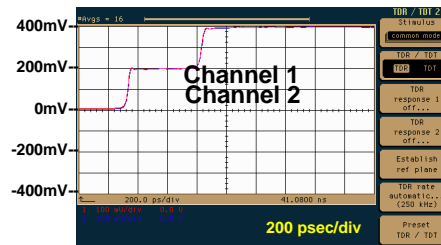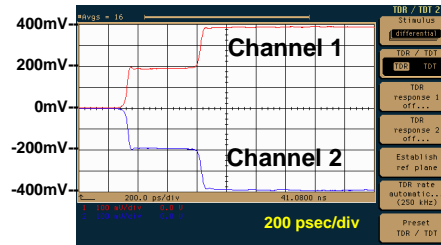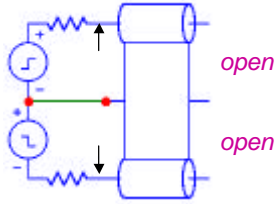

© Eric Bogatin 2000

www.BogatinEnterprises.com



Measuring Odd and Even Impedance of Tightly Coupled Lines

Measured Impedance of one trace, as the other is driven:

Odd mode impedance: differentially driven pair

Even mode impedance: commonly driven pair


For identical lines

$$Z_{11} = \frac{1}{2} (Z_{\text{even}} + Z_{\text{odd}})$$

$$Z_{12} = \frac{1}{2} (Z_{\text{even}} - Z_{\text{odd}})$$


Extracted
Characteristic
impedance matrix

48.5 3.5
3.5 48.5

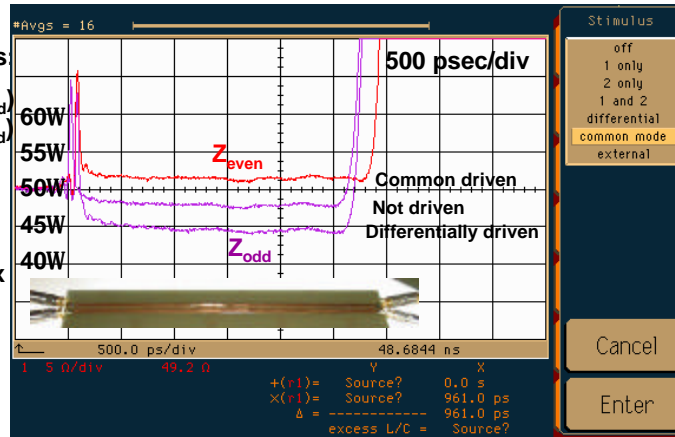


Direct Measurement of Differential Impedance
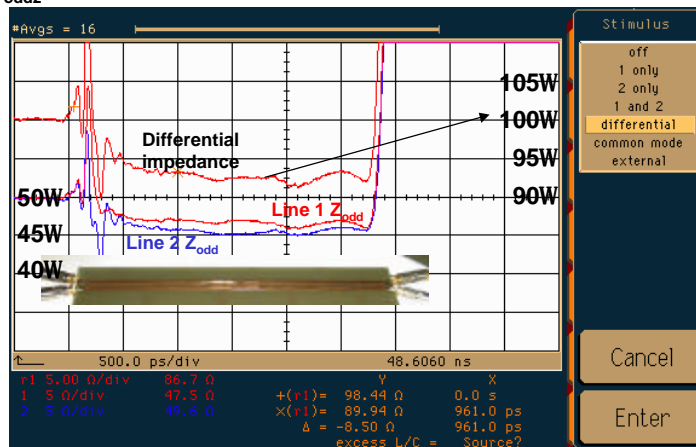
$$Z_{\text{diff}} = Z_{\text{odd1}} + Z_{\text{odd2}}$$





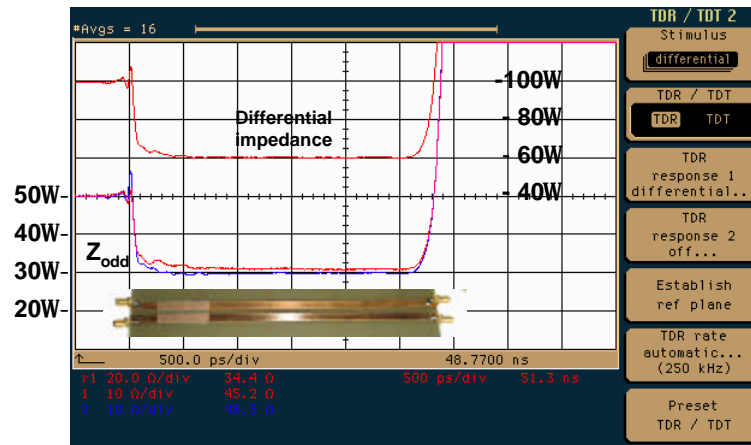
Measuring Differential Impedance of Low Impedance Traces



© Eric Bogatin 2000

www.BogatinEnterprises.com

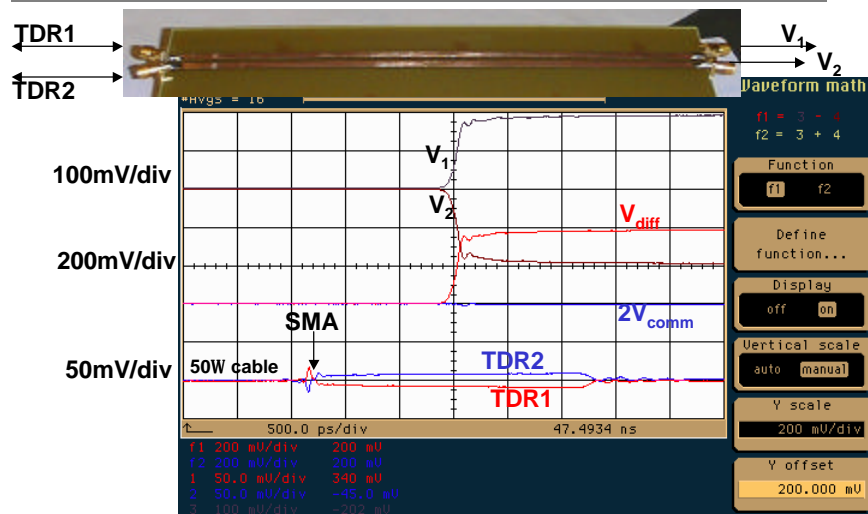Full Characterization of a Differentially Driven, Differential Pair




© Eric Bogatin 2000

www.BogatinEnterprises.com



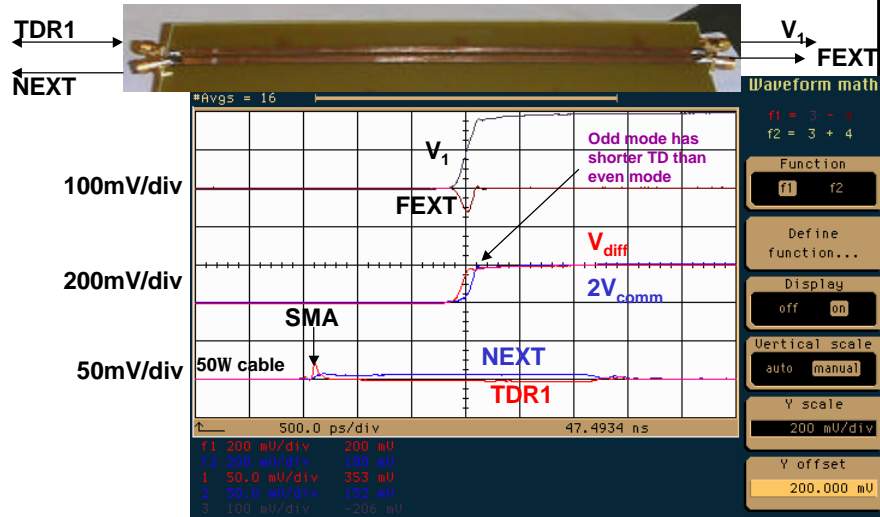
Full Characterization of a Single End Driven, Differential Pair



© Eric Bogatin 2000

www.BogatinEnterprises.com

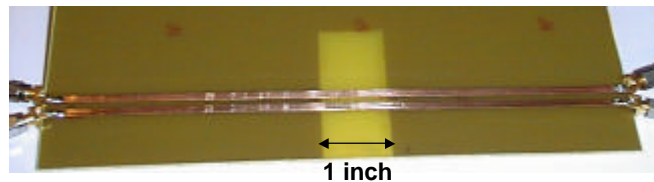Differential Pair Over Split in the Return Path



What will be the behavior when:


- single end driven
- differentially driven?

© Eric Bogatin 2000

www.BogatinEnterprises.com



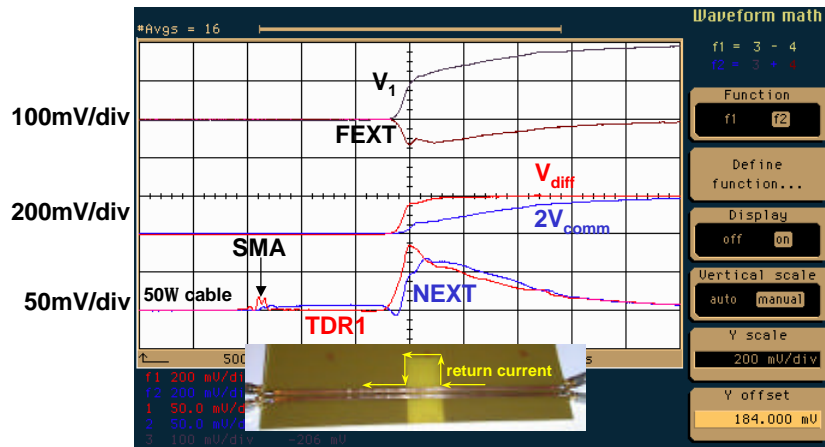
Full Characterization of a Single End Driven, Differential Pair Over a Split in the Return Path



© Eric Bogatin 2000

www.BogatinEnterprises.com

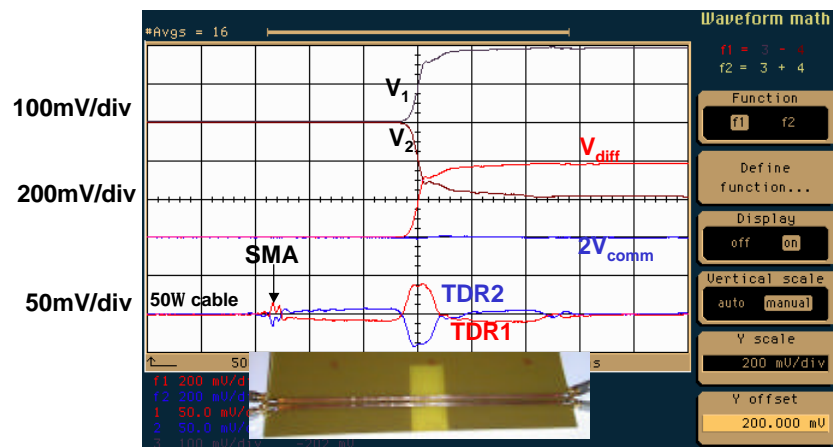Full Characterization of a Differentially Driven, Differential Pair Over a Split in the Return Path




© Eric Bogatin 2000

www.BogatinEnterprises.com



Measured Impedances

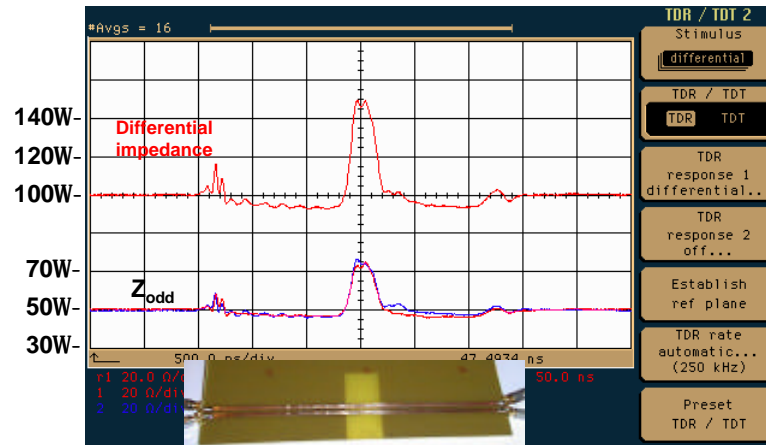


© Eric Bogatin 2000

www.BogatinEnterprises.com


Impedance as the Dielectric Thickness Increases



Ansoft Maxwell 2D Extractor

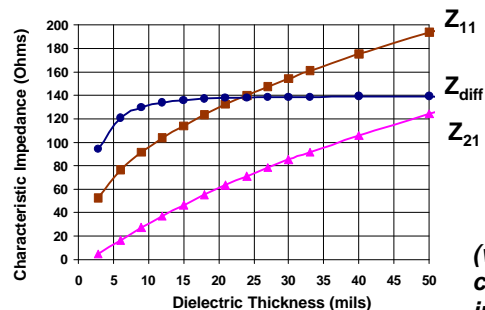

Ansoft Maxwell 2D Extractor



$Z_{diff} \sim 140$ Ohms with the bottom plane as the return path, when far away


(when Z_{21} is a large fraction of Z_{11} , coupling dominates, differential impedance approaches single ended impedance)

© Eric Bogatin 2000

www.BogatinEnterprises.com



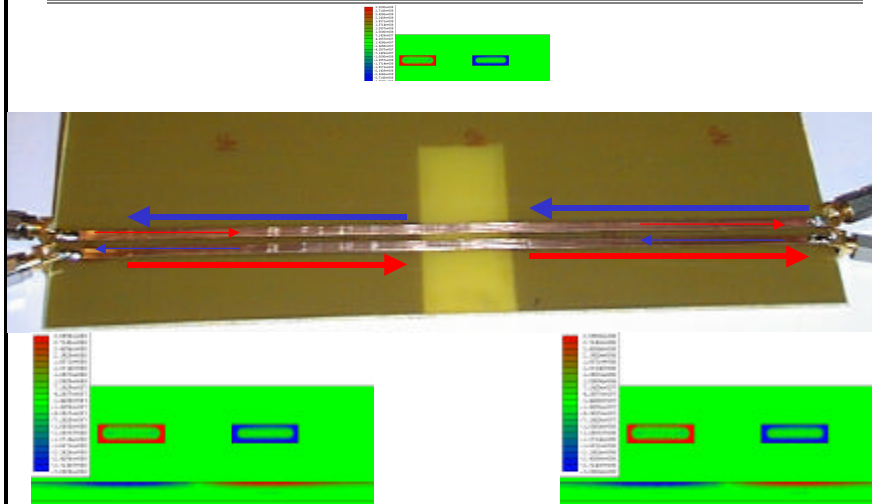What Are the Return Currents When Driven Differentially?




© Eric Bogatin 2000

www.BogatinEnterprises.com

Return Currents in Differential Pairs


Most return current is carried by the plane when trace to plane coupling >> trace to trace coupling

Ex: most board level interconnects

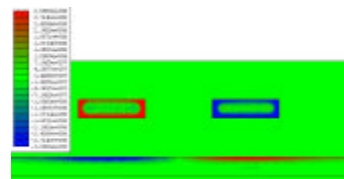

Most return current is carried by the other trace when trace to plane coupling << trace to trace coupling

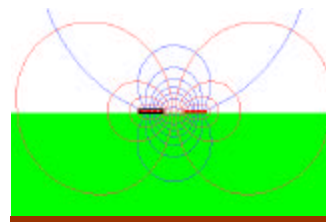Ex: most connectors, shielded twisted pair, twisted pair



© Eric Bogatin 2000



www.BogatinEnterprises.com



First Order Approximations to Differential Impedance: Microstrip

$$Z_{diff} = 2Z_0 \left(1 - 0.48 \exp \left(-0.96 \frac{s}{h} \right) \right)$$

National Semiconductor model
Apnote 905

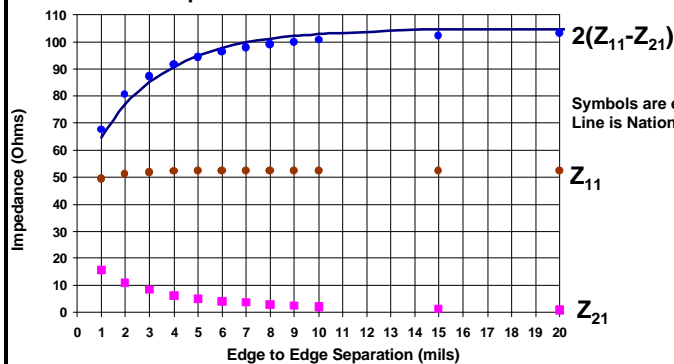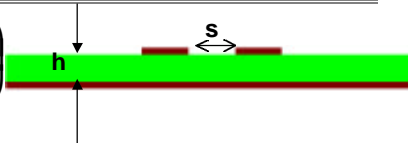



Symbols are extracted with field solver
Line is National model



First Order Approximations to Differential Impedance: Stripline

$$Z_{diff} = 2Z_0 \left(1 - 0.347 \exp \left(-2.9 \frac{s}{b} \right) \right)$$

National Semiconductor model
Apnote 905

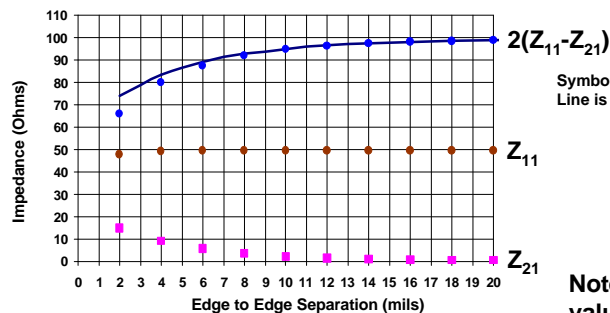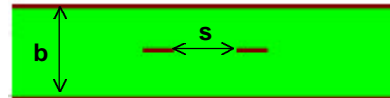

Symbols are extracted with field solver
Line is National model




Note, accurate only for Z_0
values near 50 Ohms!




Impact from Width of the Line

$b = 15$ mils
 $s = 5$ mils
 Sweeping w

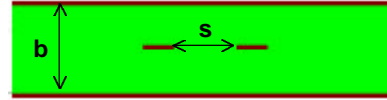

National
 Semi
 model


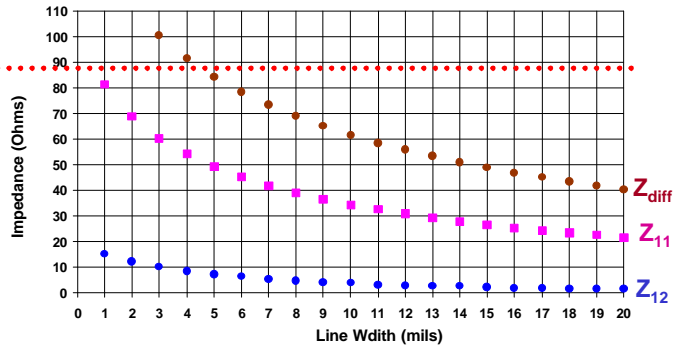


© Eric Bogatin 2000

www.BogatinEnterprises.com


Shielded Twin Leads, Changing Shield Size

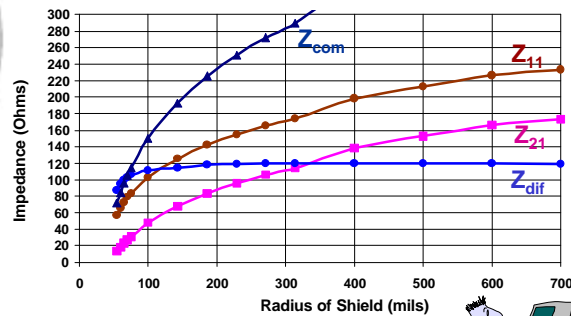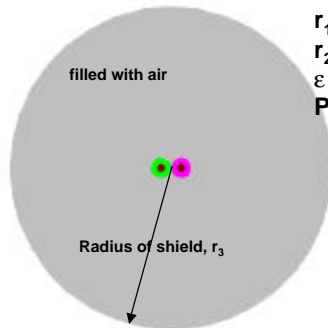$r_1 = 10$ mils
 $r_2 = 25$ mils
 $\epsilon = 4$
 Pitch = 50 mils
 Single ended impedance = 120W



**differential impedance approaches single
 ended impedance when $r_s > 3 \times \text{pitch}$**

Ansoft Maxwell 2D Extract

© Eric Bogatin 2000

www.BogatinEnterprises.com



Summary

- The impedance of one line in a differential pair depends on how the other is being driven:
 - ✓ Measure odd impedance by driving differentially
 - ✓ Measure even impedance by driving in common
 - ✓ Requires Differential TDR (DTDR)
- Characteristic impedance matrix elements can be extracted from odd and even impedances
- A gap in the return path causes huge increase in cross talk in single ended lines due to high mutual inductance
- If you must cross a split plane, better to use a diff pair
 - ✓ Some increase in differential impedance
 - ✓ Very little distortion of differential signal
 - ✓ Very little common voltage created
- Full characterization of differential pairs is possible with DTDR and dual channel amplifier module



***For more information on resources
and references, visit our web site:***

www.BogatinEnterprises.com